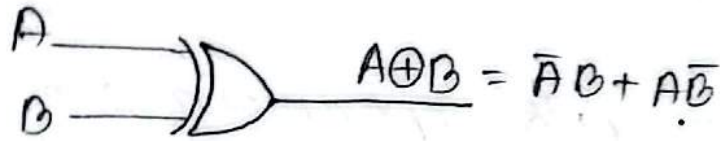
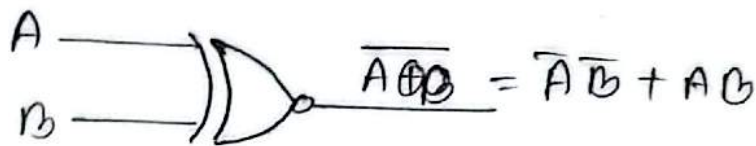


X-OR:X-NOR:Truth table: (X-OR)

in		out		
A	B	$\bar{A}B$	$A\bar{B}$	$A \oplus B$
0	0	0	0	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

(HW)

• X-OR & X-NOR gate are

~~the~~ truth table

produce same output

• $A \oplus B \oplus C$ & $\overline{A \oplus B \oplus C}$ are

~~the~~ 2/21